

# Assignment 1

Wednesday, October 8, 2025 2:05 PM

A three-phase two-level VSC is connected to a constant DC voltage source on its DC-side, and its AC-side is connected to an infinite bus through an LR filter. The VSC system has the following specifications:

- Grid voltage: 580 V (line-to-line, RMS)  $= V_{LL,RMS}$
- Grid frequency: 60 Hz
- DC-link voltage: 1000 V
- Rated power: 100 kVA  $= S_{base}$
- Modulation strategy: Sinusoidal PWM
- Control mode: GFL PQ control
- Switching frequency: 3.06 kHz

For all subsequent questions, you may use any design procedure to obtain your controller parameters. Bode plots, root locus, MATLAB SISOTOOL, Nyquist plot, state-space designs are all accepted, but trial-and-error methods are not acceptable.

You do not need to design the outer PQ controller loop: instead, divide your power set-points by grid voltage to obtain inner current controller references.

You can simulate the VSC system in either MATLAB/Simulink, PSCAD, or PLECS. Converter latency and higher-order harmonics can be neglected.

1. [10 points] Design the LR filter values for the VSC, using the procedure developed in class. Then use these values in all subsequent questions.

$$S_{base} = 100 \text{ kVA} \quad \omega_0 = 2\pi \cdot 60 = 376.99$$

$$V_{LL,RMS} = 580 \text{ V}$$

$$Z_{base} = \frac{V_{LL,RMS}^2}{S_{base}} = R_{base} = X_{base} = \frac{580^2}{100 \cdot 10^3} = 3.364 \text{ } \Omega$$

$$L_{base} = \frac{X_{base}}{\omega_0} = \frac{3.364}{376.99} = 8.9 \text{ mH}$$

$$\bullet L \sim 10\% - 20\% \text{ of } L_{base}$$

$$\Rightarrow L = 0.15 L_{base} = 0.15 (8.9 \text{ mH}) = 1.3 \text{ mH} \quad 3e^{-3}$$

$$\bullet \text{Quality factor: } Q = \frac{\omega_0 L}{R} = \frac{X_L}{R} \Rightarrow \text{ideally } Q > 75\%$$

$$\bullet \text{calculate } R = \frac{\omega_0 L}{Q}$$

$$\hookrightarrow \text{set } Q = 75 = 37.5$$

$$\Rightarrow R = L = 1.3 \text{ m}\Omega$$

2. [40 points] Design PI current controller and PLL controller for the VSC, using the net control block diagram models developed in class.

- a. Show your detailed design procedure for **current controller** (e.g., provide bode plot/root locus plot of your system, any calculations you have done, and/or any code, and explain why you have chosen the final controller parameters) and provide the final

$$\text{PI controller design in the format of } C(s) = k_p + \frac{k_i}{s}$$

$$\text{loop gain: } L(s) = \left( \frac{K_f}{L_s} \right) \frac{s + \frac{K_i}{K_f}}{s + R/L} \Rightarrow L(s) = \frac{K_f}{L_s}$$

$$\text{Closed-loop transfer function: } \frac{i_d(s)}{i_d^{ref}(s)} = G_i(s) = \frac{1}{L_i s + 1}, \text{ choose } \begin{matrix} \text{proportional gain} \\ \downarrow \\ K_f = \frac{L}{L_i} \end{matrix} \quad \begin{matrix} \text{integral gain} \\ \downarrow \\ K_i = \frac{R}{L_i} \end{matrix}$$

$$\bullet \text{Choose } L_i \text{ so it's small for fast current controller response, but large enough s.t. } \frac{1}{L_i} \text{ (b.w.)}$$

is about  $10\times$  smaller than switching frequency ( $f_{sw} = 3.04 \text{ kHz}$ )


$$\Rightarrow \tau_i = 3 \text{ ms} \rightarrow \frac{1}{\tau_i} \sim 0.3 \text{ kHz}$$

$$K_P = \frac{L}{\tau_i} = \frac{1.3 \text{ mH}}{3 \text{ ms}} = 0.43 \text{ [V/A]}$$

$$K_I = \frac{R}{\tau_i} = \frac{1.3 \Omega}{3 \text{ ms}} = 0.43 \text{ [V/A]}$$

$$G(s) = 0.43 + \frac{0.43}{s}$$

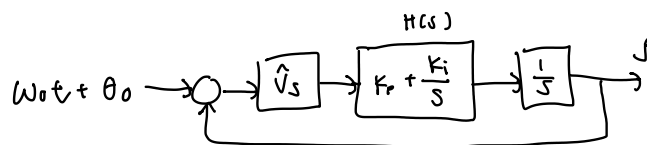- b. Show your detailed design procedure for PLL controller (e.g., provide bode plot/root locus plot of your system, any calculations you have done, and/or any code, and explain why you have chosen the final controller parameters) and provide the final PI controller design in the format of  $H(s) = k_{PLL} + \frac{k_{IPLL}}{s}$



- Goal: regulate  $V_{sq}$  at zero

$$\bullet \omega(t) = H(s) V_{sq}(t) \text{ [rad/s] / V}$$

$$\hat{V}_s = \left( \frac{580 \text{ V}}{\sqrt{3}} \right) (\sqrt{2}) = 473.6 \text{ V}$$

$$\bullet \frac{d\varphi}{dt} = H(s) \hat{V}_s \sin(\omega_0 t + \theta_0 - \varphi)$$

$$\bullet \Delta\omega = \frac{d\varphi}{dt} = H(s) \hat{V}_s (\omega_0 t + \theta_0 - \varphi)$$

- Since linearizing around steady state  $\omega_0$ ,  $\omega(0) = \omega_0$  ?  $\omega_{min} \leq \omega \leq \omega_{max}$

- $[\omega_{min}, \omega_{max}] \sim [55, 65 \text{ Hz}] \rightarrow$  close to  $\omega_0$  but not too close

- Closed-loop transfer function:  $\frac{\varphi}{\varphi_{ref}} = \frac{G(s)}{1+G(s)}$  where  $G(s) = \hat{V}_s \left( K_P + \frac{K_I}{s} \right) \left( \frac{1}{s} \right)$

$$\frac{\varphi}{\varphi_{ref}} = \frac{\hat{V}_s \left( K_P + \frac{K_I}{s} \right) \left( \frac{1}{s} \right)}{1 + \hat{V}_s \left( K_P + \frac{K_I}{s} \right) \left( \frac{1}{s} \right)} = \frac{\hat{V}_s K_P s + \hat{V}_s K_I}{s^2 + \hat{V}_s K_P s + \hat{V}_s K_I}$$

Denominator:  $s^2 + \hat{V}_s K_P s + \hat{V}_s K_I$

$$\omega_n^2 = \hat{V}_s K_I \Rightarrow \omega_n = \sqrt{\hat{V}_s K_I} \Rightarrow K_I = \frac{\omega_n^2}{\hat{V}_s}$$

damping ratio:  $\zeta = \frac{V_s K_P}{2 \sqrt{\hat{V}_s K_I}} \quad K_P = \frac{9.2 \sqrt{\hat{V}_s K_I}}{V_s}$

choosing:

$$\} \text{ Set } BW = 20 \text{ Hz} = 2 \cdot \pi \cdot 20 \text{ Hz} = 125.66 \text{ rad/s}$$

$$BW = \omega_n \left[ 1 + 2\zeta^2 + \sqrt{(1 + 2\zeta^2)^2 + 1} \right]^{1/2}$$

$$\Rightarrow \omega_n = BW \cdot \left( 1 + 2\zeta^2 + \sqrt{(1 + 2\zeta^2)^2 + 1} \right)^{-1/2}$$



$$\omega_n = 61.1 \text{ rad/s}$$

choosing:  $\xi = 0.707$


$$\Rightarrow K_i = \frac{\omega_n^2}{\xi} = \frac{(411)^2}{473.6} = 7.98$$


$$\Rightarrow K_p = \frac{(0.707)(2)(\sqrt{473.6}(7.98))}{473.6} = 0.182$$

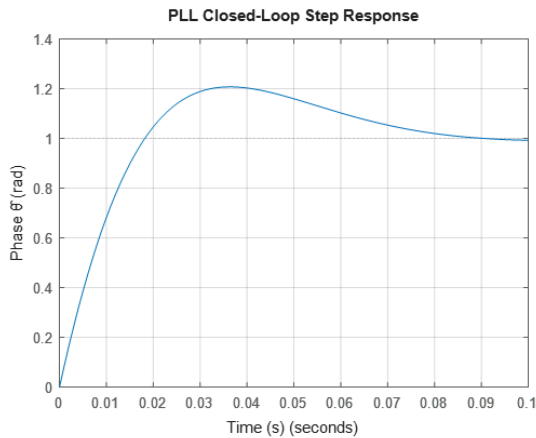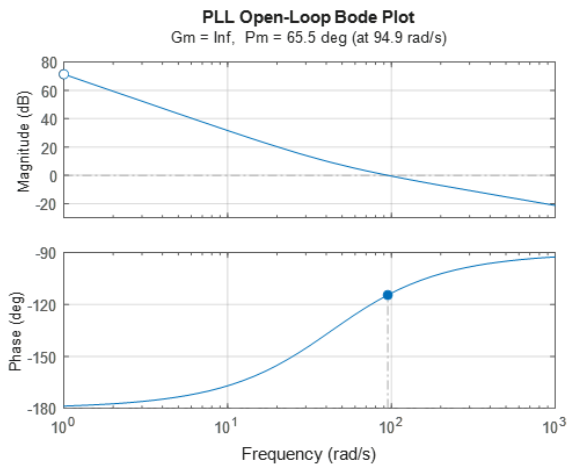Final PI control design:  $H(s) = K_{p,PI} + \frac{K_{i,PI}}{s} = 0.182 + \frac{7.98}{s}$







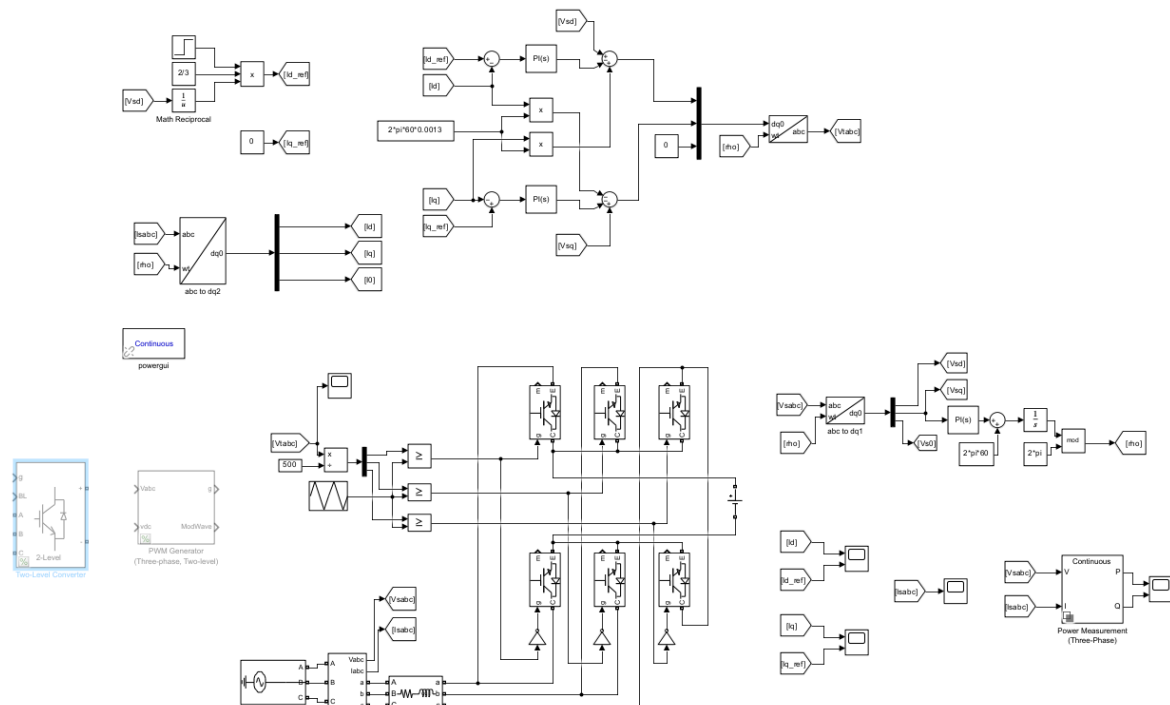
- c. Simulate the GFL VSC with your controllers: In the beginning, set both  $P^{ref}$  and  $Q^{ref}$  to 0, and subsequently, step up  $P^{ref}$  to 100 kW. Plot the following and briefly comment on the results (make sure you plot the waveforms for a total of 6 cycles, i.e., 2 cycles before step change and 4 cycles after step change)
- $i_d$  and  $i_d^{ref}$  on the same plot
  - $i_q$  and  $i_q^{ref}$  on the same plot
  - 3-phase AC currents on the same plot
  - Measured real and reactive powers at the PCC on the same plot



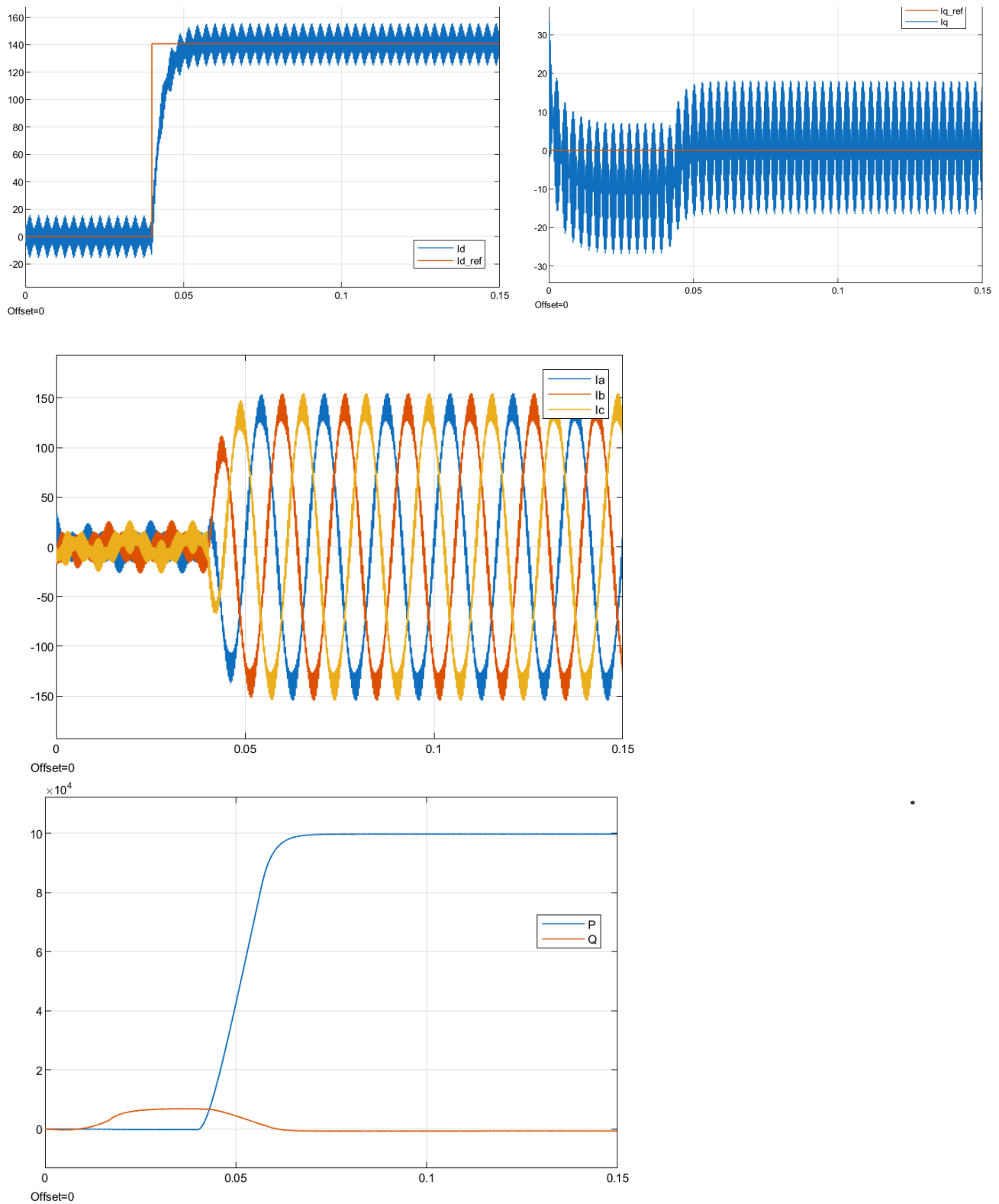

- $I_d$  shows that it quickly catches up to  $I_{dref}$  after the disturbance after about 0.01s. There is noise in  $I_d$ , but the measurements are stable around the new  $I_{dref}$ .
- Before the disturbance,  $I_q$  averages a value slightly below  $I_{qref}$  (which is zero). After the disturbance,  $I_q$  seems to follow the reference better at zero. The fact that  $I_q$  seems to be affected by the real power step up shows that  $I_q$  and  $I_d$  are not completely decoupled- however, it does not seem to affect the accuracy of  $I_q$ .
- The three phase abc currents increase in amplitude after the step up of the real power.
- The real power reflects the step up that we are inducing at 0.04s. The Q value stays at zero after the real power steps up, as reactive power should be unaffected.

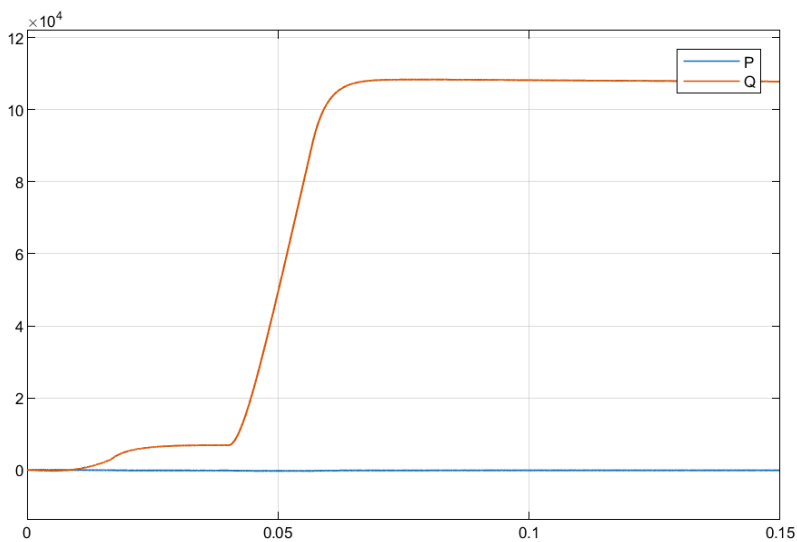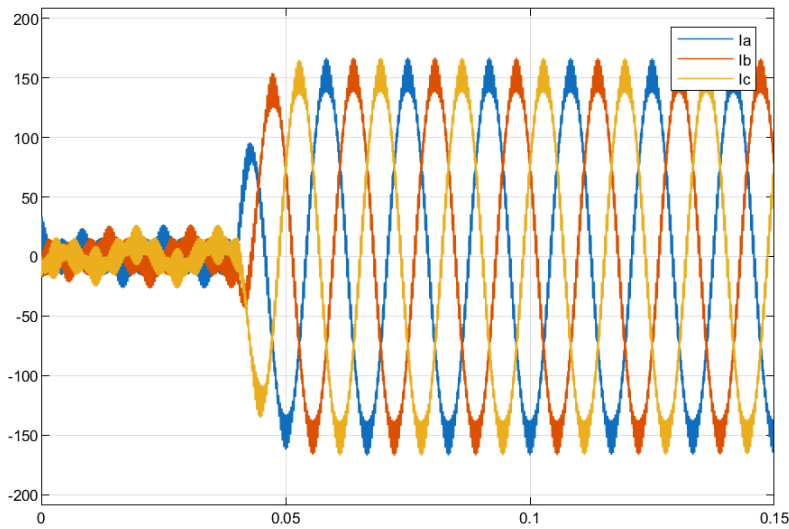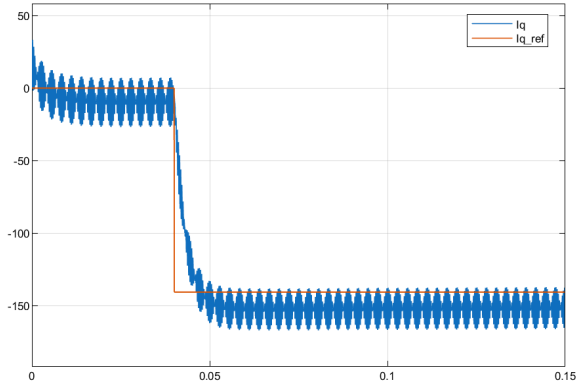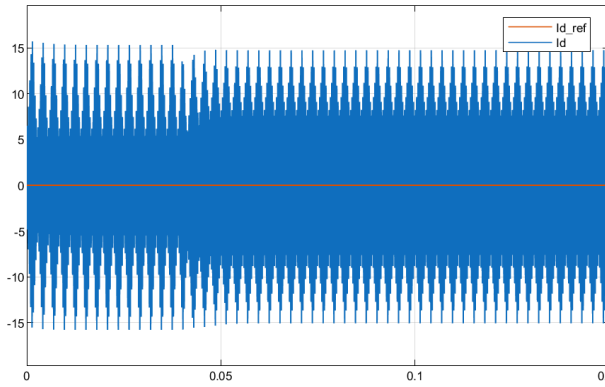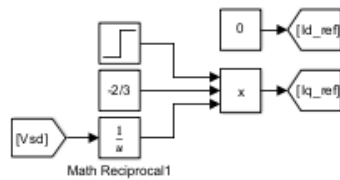d. Repeat part (c) with a step change of 100 kVAr in reactive power exchange








- i. Id does not seem to be affected by the disturbance, meaning Id and Iq are well decoupled. Id maintains an average around 0, following Idref.


- ii.  $I_{qref}$  sees a step down from the increase in reactive power  $Q$ .  $I_q$  follows  $I_{qref}$ , except that the average of  $I_q$  is slightly lower than  $I_{qref}$ .
- iii. The three phase abc currents increase in amplitude after the step up of the reactive power.
- iv. The reactive power reflects the step up that we are inducing at 0.04s. The  $P$  value stays at zero after the reactive power steps up, as real power should be unaffected.

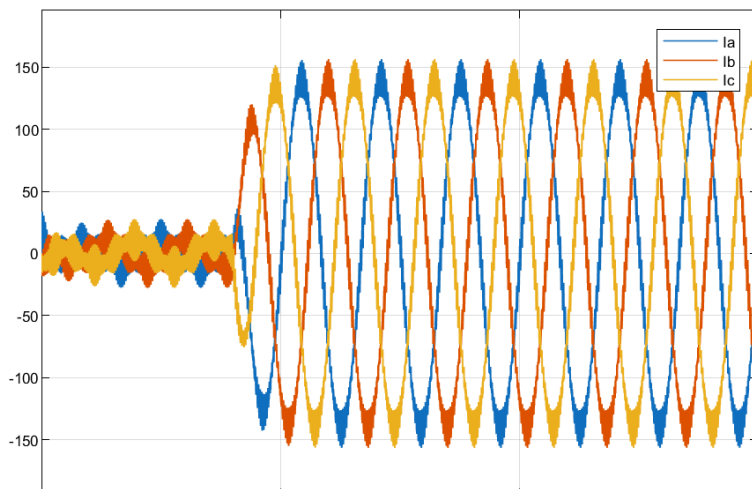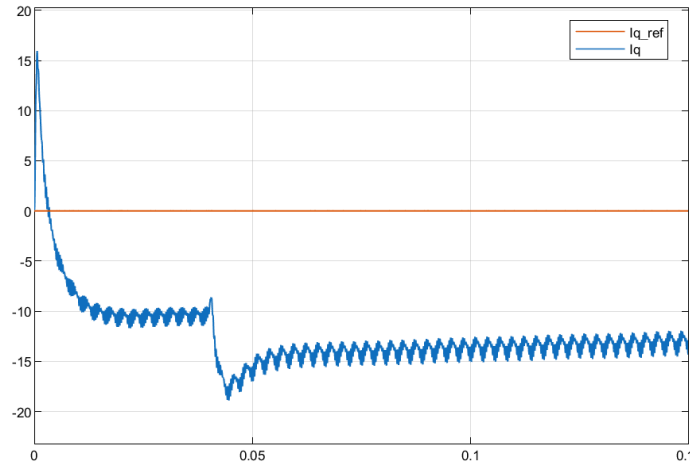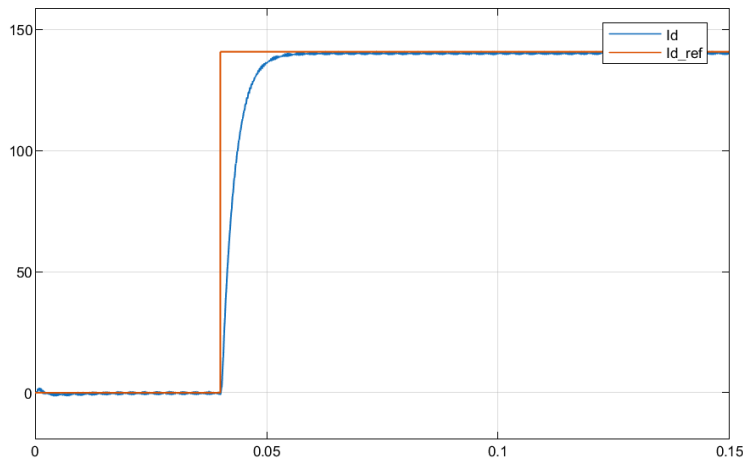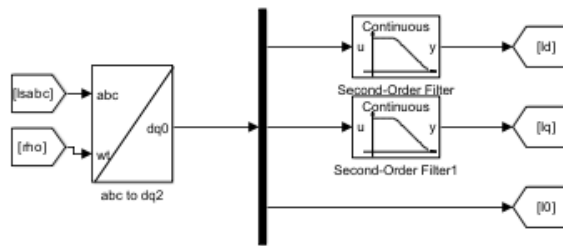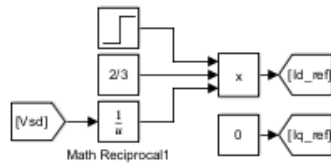3. [40 points] Repeat question (2) by placing second order low-pass filters on the  $i_{dq}$  measurements. The filter has a unity gain,  $\omega_n = 5000 \text{ rad/s}$ ,  $\zeta = 0.8$ , with an expression of




$$L(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



Keep in mind that there is no need to (i) re-design LR filter and (ii) re-design PLL controller again for this question.



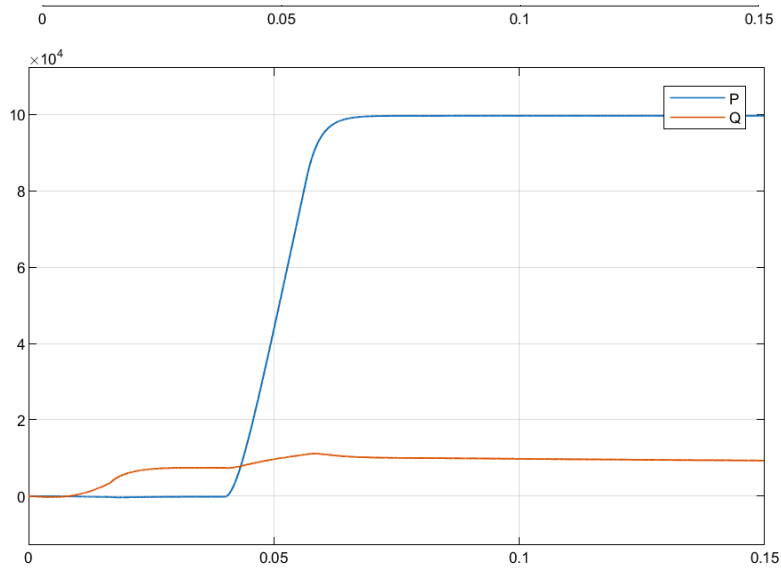

- $I_d$  follows  $I_{dref}$  well and the addition of the low-pass filter smooths out the noise in  $I_d$  well.
- With the addition of the low-pass filter,  $I_q$  does not follow  $I_{qref}$  as well and is slightly lower than  $I_{qref}$ . However, it is constant after the disturbance and with less noise than without the filter.
- There is not any noticeable difference in  $I_{abc}$  after adding the low-pass filter. This makes sense as  $I_d$  and  $I_q$  are filtered, not  $I_{abc}$ .
- The real power reflects the step up that we are inducing at 0.04s, however, with the addition of the filter, the reactive power  $Q$  increases above 0 and stays constant after the disturbance. This could indicate some filter delay that is causing incorrect decoupling between  $I_d$  and  $I_q$ .

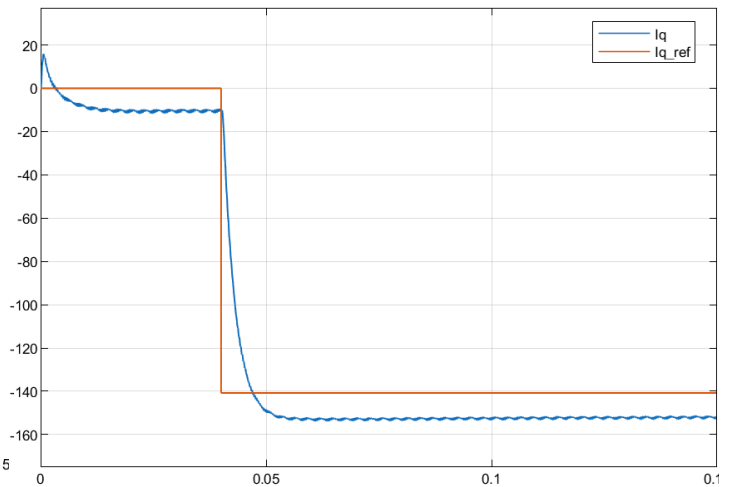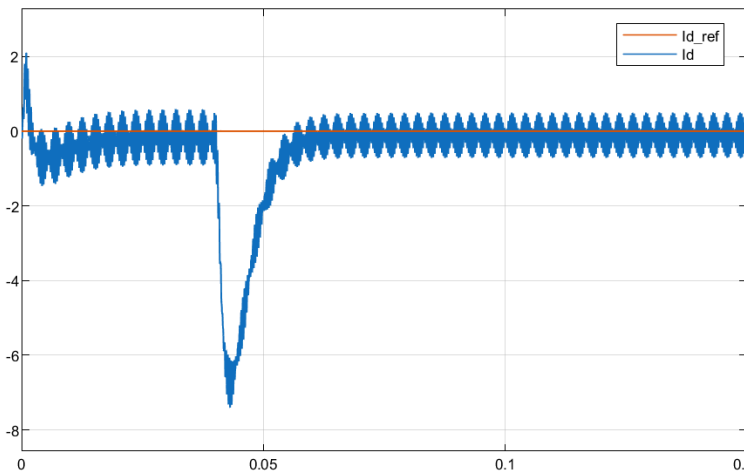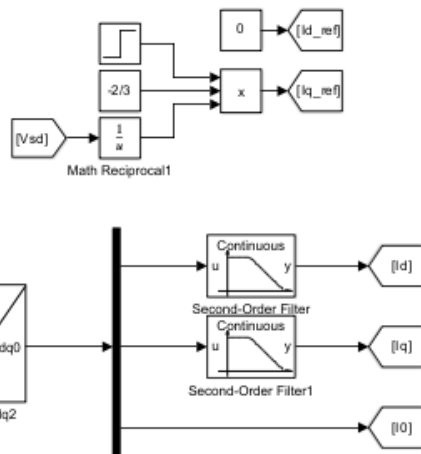

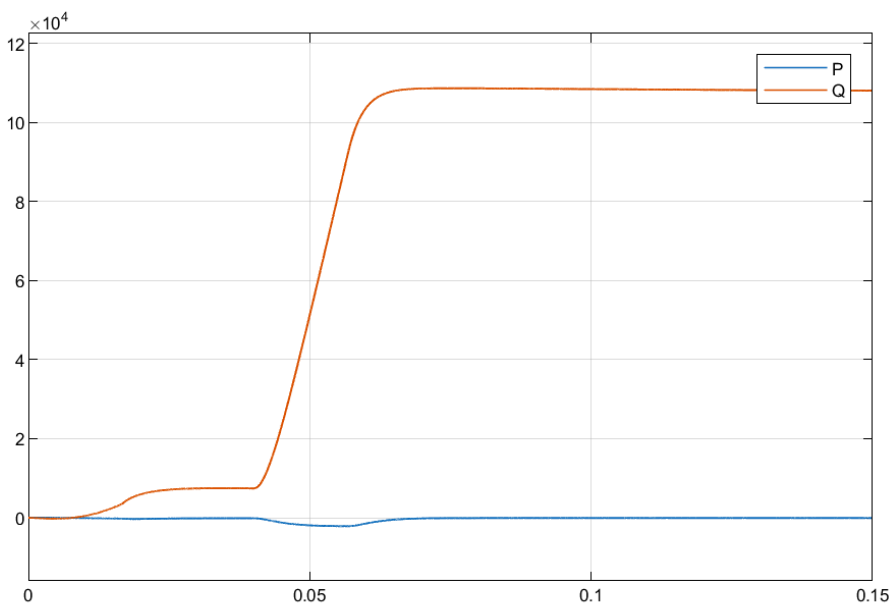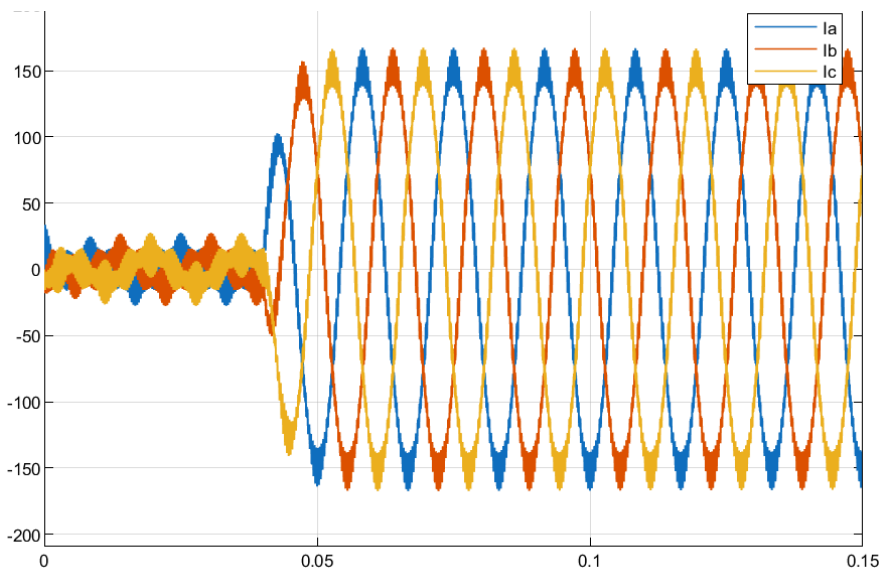

- i.  $I_d$  follows  $I_{dref}$  before and after the step up in  $P$ , but there is a noticeable dip when the step up occurs. This indicates incorrect decoupling in the current controller.
- ii. With the addition of the low-pass filter,  $I_q$  is much less noisy, however, the value of  $I_q$  is slightly off from  $I_{qref}$ .
- iii. There is not any noticeable difference in  $I_{abc}$  after adding the low-pass filter. This makes sense as  $I_d$  and  $I_q$  are filtered, not  $I_{abc}$ .
- iv. The reactive power reflects the step up that we are inducing at 0.04s and the real power maintains a constant zero.

4. **[10 points]** For the 3-phase system shown in class ( $\text{gnd} - V_t - L - R - V_s - \text{gnd}$ ), we showed that  $[V_{s\alpha\beta 0}] = R[i_{\alpha\beta 0}] + L \frac{d}{dt}[i_{\alpha\beta 0}] + [V_{t\alpha\beta 0}]$ , where  $R$  and  $L$  are scalars. How, if at all, does this formulation change if  $V_s$  is unbalanced?

If  $V_s$  is unbalanced, negative sequence and possibly zero sequence exist.

However,  $\begin{bmatrix} V_\alpha \\ V_\beta \\ V_0 \end{bmatrix} = [C] \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$  is still maintained, it's just that  $V_0$  has a



nonzero value.

so in a balanced system,  $[V_{s\alpha p}] = [V_{s\alpha p}]$ , but in the unbalanced system,

$[V_{s\alpha p}] \neq [V_{s\alpha p}]$  and so we cannot get rid of the 0 term.

$$V_{s\alpha} = R_{i\alpha} + L_{i\alpha} + V_{t\alpha}$$

$$V_{sp} = R_{ip} + L_{ip} + V_{tp}$$

$$V_{so} = R_{io} + L_{io} + V_{to}$$